
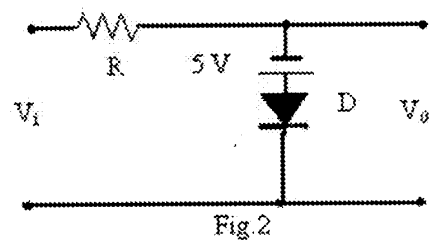


Baskent University, Faculty of Engineering
BME 222-02 – Electronics (Spring Semester 2004/2005)
Quiz 1 – March 25, 2005

Student Name _____

Faculty No: _____

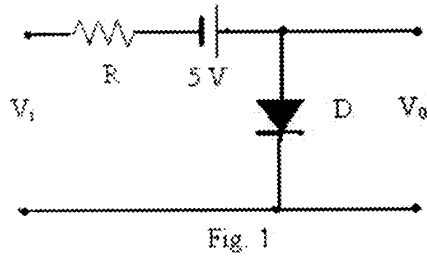


Determine the output V_o for the networks of Fig. 1, 2, if the input V_i is sinusoidal signal with peak-to-peak magnitude of 20 V, and frequency of 1000 Hz. Assume ideal diodes.

5 points.

Good Luck!

Solutions

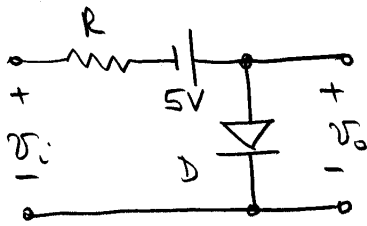

1. Transition level:



$$-v_i + V_R - 5 + V_D = 0$$

$$V_D = 0; I_D = 0; V_R = 0$$

$$-v_i = 5V; v_i = -5V$$

2. $v_i = 10V; v_o = 0V$

$v_i = -10V; v_o = -5V$

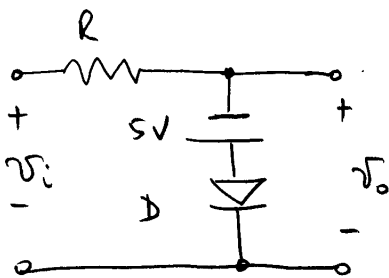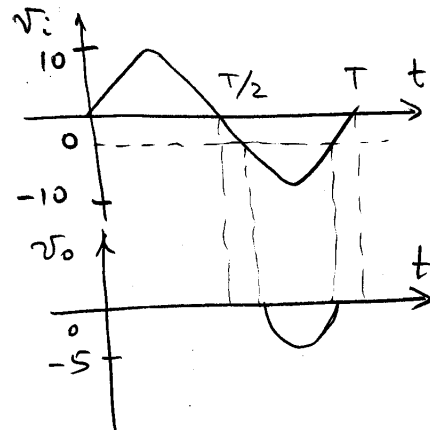

1. Transition level:

$$-v_i + V_R - 5 + V_D = 0$$

$$V_D = 0; I_D = 0$$

$$V_R = 0$$

$$v_i = -5V$$

2. $v_i = 10V; v_o = -5V$

$v_i = -10V; v_o = -10V$

