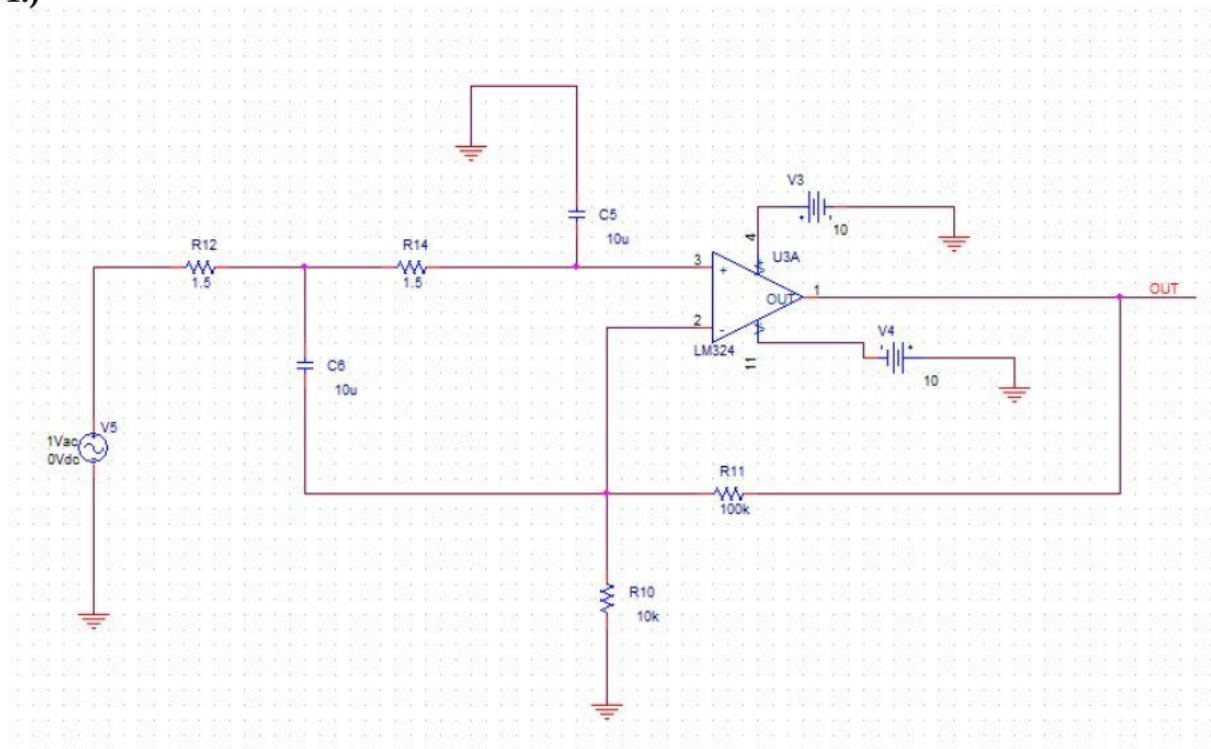


EXPERIMENT 8 ACTIVE FILTERS

PRELIMINARY WORK:


1.)



$f = 3\text{kHz}$ $C = 10\mu\text{F}$ ise;

$R = 375.131\text{k}\Omega$

2.)

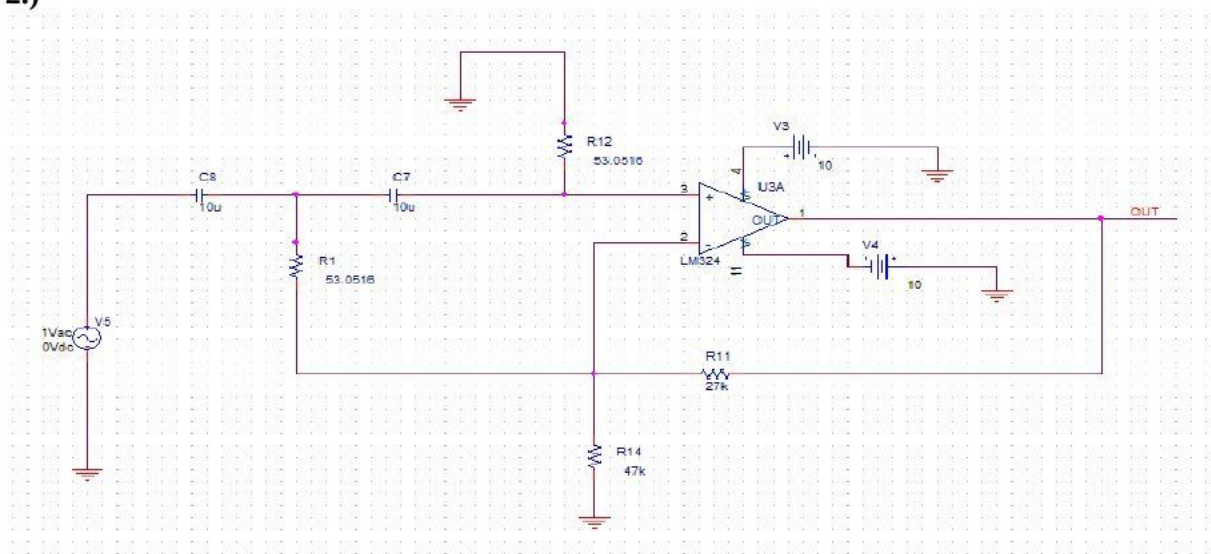

$f = 300\text{ Hz}$ $C = 10\mu\text{F}$ ise;

$R = 53.0516\Omega$

3.)

