

EEM 214 ELECTRONICS
LABORATORY#3
PRELIMINARYWORK

- 1) Find the mode of these transistors (active, cut off, saturation) ? If they are in active mode find the Q-points of the transistors ? ($\beta=100$, $V_{BE}=0.7$)

